

①

must be known:

- numbers and number systems
- Arithmetics
- Coding BCD, XS-3, gray
- (+) and (-) numbers and their representations in any base
- Laws of Boolean algebra
- Simplification of switching functions using algebraic manipulations.
- Basic idea about the design procedure of combinational ckt's.

<u>S</u>	<u>K</u>	<u>S</u>	<u>T</u>
7.55	7.35	7.30	8.10
9	8.30	8.30	9
10.15	9.45	9.30	10
11.15	10.45	10.30	12
11.45	12	12.30	13.45
12.45	12.45	14.15	15.45
14.15	13.45	16.15	16.45
15.15	14.45	17.30	19
16.15	15.45	19.30	20
17.15	16.45	20.30	22
18.15	17.45	22.30	23.15
20	19.30	23.45	
21	22		

Summary of the course

- Combinational ckt's.
- Hazards in Comb. ckt's.
- MT1 - Analysis and synthesis of synchronous switching ckt's.
- MT2 - Analysis and synthesis of asynchronous swt. ckt's.

References

- Logical design of digital systems. Donald Diethage.
- Introduction to switching theory and logical design. Hill and Peterson.
- Switching and finite automata. Z. Kohavi.
- Mano

07101980

Example: given $B = \{1, 3\}$ together with the operations $\forall a, b$ in B . $a + b \equiv$ The least common multiple of a and b . ($\max a, b$) $a \cdot b \equiv$ The greatest common divisor ($\min a, b$)

$$a' = \frac{3}{a}$$

Check whether satisfies the laws of Boolean algebra:

<u>+</u>	<u>1</u>	<u>3</u>	<u>.</u>	<u>1</u>	<u>3</u>	<u>a</u>	<u>a'</u>
1	1	3	1	1	1	1	3
3	3	3	3	1	3	3	1

A1 - Commutativity holds. (Can be seen through the tables)

A2 -

$$\begin{array}{ll}
 1+1=1 & 3+1=3 \\
 1 \cdot 3=1 & 3 \cdot 1=1 \\
 1 \cdot 1=1 & 3+3=3 \\
 1+3=3 & 3 \cdot 3=3
 \end{array}
 \rightarrow
 \begin{array}{l}
 1_+ \equiv 1 \\
 1_\cdot \equiv 3
 \end{array}$$

$$\begin{array}{l}
 1_\cdot \cdot a = a \\
 1_+ + a = a
 \end{array}$$

$$1_\cdot + a = 1_\cdot$$

$$1_+ \cdot a = 1_+$$

A3 - $a + (b \cdot c) = (a+b) \cdot (a+c)$

Set $a = 1$

$$\underbrace{1 + (b \cdot c)}_{b \cdot c} = \underbrace{(1+b)}_b \cdot \underbrace{(1+c)}_c$$

(look at the table)

$$= b \cdot c$$

Set $a = 3$

$3 + (b \cdot c) = (3+b) \cdot (3+c)$

$3 = 3 \cdot 3$

$3 = 3$

Check: $a \cdot (b+c) = a \cdot b + a \cdot c$

\Rightarrow A3 holds.

A4 -

$$\begin{cases} a + a' = i_0 \\ a \cdot a' = i_+ \end{cases} \begin{cases} i_0 = 3 \\ i_+ = 1 \end{cases}$$

Set $a = 1$

$1 + 3 = 3 (= i_0)$

$1 \cdot 3 = 1 (= i_+)$

Set $a = 3$

$3 + 1 = 3 (= i_0)$

$3 \cdot 1 = 1 (= i_+)$

Exercise

$B = \{1, 2, 3, 6\}$


$a + b \equiv$ given previous ex.
 $a \cdot b \equiv$

$a' = \frac{b}{a}$

Switching algebra:

if there is a transmission between points A and B = 1
" " " no " " " " " = 0


1. Normally open contact:

 


2. Normally closed contact:



If two contacts are connected in series;

 


1 means energizing
0 means de-energizing

 

P	q	T _{AC}
0	0	0
0	1	0
1	0	1
1	1	0

$T_{AC} = P \cdot q'$


Transfer contact:

 


Same relay coil controls both of the contacts.

When $x = 0$
 $T_{AB} = 0$
 $T_{AC} = 1$
 $x = 1$
 $T_{AB} = 1$
 $T_{AC} = 0$
 \downarrow
 $T_{AB} = x$
 $T_{AC} = x'$

Example

 

$T_{AB} = ?$

 


$$T_{AB} = x \cdot y' + (x' + y) \cdot z'$$


$$= xy' + (xy)'.z'$$

$$\quad \underbrace{\hspace{2cm}}_{a + a'b}$$

$$= xy' + z'$$

 

Example

 

$l = 0$ OFF
 $l = 1$ ON

$l = 0$ when $x_1, x_2, x_3 = 0$
 $l = 0$ when any two of switches are 1
 $l = 1$ when only one of the switches is 1
 $l = 1$ when all the switches are 1

x_1	x_2	x_3	l	l'
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0

Canonical sum-of-products (CSP)
Expression

$$l = x_1'x_2'x_3 + x_1'x_2x_3' + x_1x_2'x_3' + x_1x_2x_3$$

Canonical product-of-sums (CPS)
Expression

$$l' = x_1'x_2'x_3' + x_1'x_2x_3 + x_1x_2'x_3 + x_1x_2x_3'$$

$$(l')' = l = (x_1 + x_2 + x_3)(x_1 + x_2' + x_3')(x_1' + x_2 + x_3')(x_1' + x_2' + x_3)$$

Definition: With an 'n' variable switching function, the form

$$m_k = x_1 x_2 x_3 \dots x_n \text{ is called a minterm.}$$

Definition: An expression containing only minterms is called canonical sum-of-products (CSP) expression.

→ if the # of and order of the variables are known m_k has a unique meaning.

$n = 3$ abc order: cab

$$m_6 = cab' = abc'$$

13/10/1980

Canonical sum of product = canonical minterm expression:

$$f(x_1, x_2, \dots, x_n) = \sum_{i=0}^{2^n-1} \alpha_i m_i$$

n : # of variables
 m_i : i th minterm
 α_i : either 0 or 1

example: $n = 3$

$$f(x_1, x_2, x_3) = \sum_{i=0}^7 \alpha_i m_i = \alpha_0 m_0 + \dots + \alpha_7 m_7$$

where $m_0 = x_1'x_2'x_3'$
 $m_1 = x_1'x_2'x_3$

Definition: An expression of the form (for n variable function)

$M_k = (x_1 + x_2 + \dots + x_n)$ is called a maxterm.

x_i is the i th variable in primed or unprimed form. The expression of the function f in the form:

$$f(x_1, x_2, \dots, x_n) = \prod_{i=0}^{2^n-1} (\alpha_i + M_i) \text{ is called canonical product of sum expression "maxterm"}$$

$n = \#$ of variables

$M_i = i$ th maxterm

$\alpha_i =$ coefficient of maxterm (either 0 or 1)



example

	x_1	x_2	x_3	f	f'
7	0	0	0	0	1
6	0	0	1	1	0
5	0	1	0	1	0
4	0	1	1	0	1
3	1	0	0	0	1
2	1	0	1	0	1
1	1	1	0	1	0
0	1	1	1	0	1

maxterm expression:

$\alpha_6, \alpha_5, \alpha_1$ are 1 all the others are zero

$$f(x_1, x_2, x_3) = (\alpha_0 + M_0)(\alpha_1 + M_1)(\alpha_2 + M_2)(\alpha_3 + M_3)(\alpha_4 + M_4)(\alpha_5 + M_5)(\alpha_6 + M_6)(\alpha_7 + M_7)$$

$$f' = x_1'x_2'x_3' + x_1x_2x_3 + x_1x_2x_3' + x_1x_2'x_3 + x_1x_2'x_3'$$

$$(f')' = (x_1 + x_2 + x_3)(x_1 + x_2' + x_3')(M_3)(M_2)(M_0)(\alpha_6 + M_6)(\alpha_5 + M_5)(\alpha_1 + M_1)$$

$1 + m = 1$ drop these terms.

Definition: The maxterm M_k has a unique meaning if

a) # of variables

b) order of variables are given

$$2^n - 1 \geq k \geq 0$$

example: Variables: A, B, r, q

$$M_9 = (A + B' + r' + q)$$

$$9 = 1001$$

Theorem: - for an n variable function CSP expression is unique.

Shannon's expansion:

any function with n variables can be written as,

$$1) f(x_1, x_2, \dots, x_n) = x_i f(x_1, \dots, x_{i-1}, 1, x_{i+1}, \dots, x_n) + x_i' \cdot f(x_1, \dots, x_{i-1}, 0, x_{i+1}, \dots, x_n)$$

$$2) f(x_1, x_2, \dots, x_n) = [x_i + f(x_1, x_2, x_3, \dots, x_{i-1}, 0, x_{i+1}, \dots, x_n)] [x_i' + f(x_1, x_2, \dots, x_{i-1}, 1, x_{i+1}, \dots, x_n)]$$

Successive application of Shannon's expansion (1) and (2) to a Boolean function gives CSP or CPS expression of f respectively.

1-10-1980

Example

$$f(A, B, C) = AB + C$$

apply Shannon's expansion:

$$f(A, B, C) = A[1 \cdot B + C] + A'[0 \cdot B + C]$$

$$= A\{B[1 \cdot 1 + C] + B'[1 \cdot 0 + C]\} + A'\{B'[0 \cdot 1 + C] + B[0 \cdot 0 + C]\}$$

$$= AB[1 + C] + AB'[C] + A'B'[C] + A'B[C]$$

$$= AB\{C[1 + 1] + C'[1 + 0]\} + AB'[C[1] + C'[0]\} + A'B\{C[1] + C'[0]\}$$

$$+ A'B'\{C[1] + C'[0]\}$$

$$= ABC + ABC' + A'BC + A'B'C + ABC'$$

M_7

(Conversion between CSP ↔ CPS)

$$f(x_1, x_2, \dots, x_n) = \sum_{i=0}^{2^n-1} \alpha_i M_i \rightarrow \alpha_1, \alpha_3, \alpha_5, \alpha_6, \alpha_7 \rightarrow \text{for above example}$$

$$f'(x_1, x_2, \dots, x_n) = \sum_{i=0}^{2^n-1} \alpha'_i M_i \quad (\text{take the other minterms})$$

Generalized De Morgan's law:

$$f(x_1, x_2, \dots, x_n) = \left(\sum_{i=0}^{2^n-1} \alpha'_i M_i \right)' = \prod_{i=0}^{2^n-1} (\alpha_i + M_i) = \prod_{i=0}^{2^n-1} (\alpha_i + M_{2^n-1-i})$$

↓ Maxterms

CSP → CPS :

- 1- Take the other terms which are missing in the CSP expression of f.
- 2- Subtract the index of missing terms from 2^n-1 to find M_i 's

$$m_i = M_{2^n-1-i}$$

CPS → CSP

- 1- Take the missing terms M_i 's in CPS exp.
- 2- Subtract the index i from 2^n-1 to find m_i in CSP expression.

Example :

$$f(A,B,C,D) = \prod (15, 14, 13, 10, 9, 7, 6, 5, 2, 1)$$

missing terms (maxterms) : 0, 3, 4, 8, 11, 12
 corresponding minterms : $m_{15}, m_{12}, m_{11}, m_7, m_4, m_3$

$$f(A,B,C,D) = \sum (3, 4, 7, 11, 12, 15)$$

Example - Binary full adder -



	A	B	C _i	S	C _o
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

$$S = \sum 1, 2, 4, 7$$

CSP expressions

$$C_o = \sum 3, 5, 6, 7$$

$$m_6 = ABC'_i$$

$$S = \prod (7, 4, 2, 1)$$

CPS

$$C_o = \prod (7, 6, 5, 3)$$

expressions

Minimization of Switching functions :

Definition : (Minimization) given $f(x_1, \dots, x_n)$ find another expression $g(x_1, \dots, x_n)$ which is equivalent to $f(x_1, \dots, x_n)$ and minimizes some cost criteria -

- Minimal # of terms with minimal # literals in every term in a SP-expression
- literal : variables in primed or unprimed form.

example:

$$f = x'y'z' + x'y'z + xy'z + xyz + x'yz' + xyz' = \sum(0, 1, 2, 5, 6, 7)$$

$$= x'y'(z+z') + xz(y+y') + yz' \rightarrow SP$$

$$= x'z' + y'z + yz' \rightarrow SP$$





(0,2) (1,5) (7,6)




Map method for minimization (Karnaugh map)



2²ⁿ

    


27A01980

 


3 var. Karnaugh Map. n variables \rightarrow 2ⁿ cells.

4 var. Karnaugh Map:

 

5 Variable Karnaugh Map:

 

Adjacent cells : Two cells which differ only one variable value (or the Hamming distance between them is 1) are said to be adjacent cells.
 Each cell in an n variable map has n adjacent cells.


Hamming distance : $A = a_0 a_1 \dots a_n$
 $B = b_0 b_1 \dots b_n$

$A = 011001$
 $B = 111000$ \rightarrow A and B are not adjacent.

$$H = \sum_{i=0}^n (a_i \oplus b_i)$$

(Hamming distance)
 
$$H = 1+0+0+0+1+1 = \underline{\underline{3}} \rightarrow H > 1$$



17 \rightarrow 16, 25, 19, 1, 21

Definition : A collection of 2^m (m integer) cells each adjacent to m cells of the collection is called a SUBCUBE


Each subcube can be expressed by a product term containing $n-m$ literals

n : # of variables

m : order of the subcube

A subcube is said to cover the cells belonging it.

Example :

 


18
 40% { MT1 : 25 Kasım
 MT2 : 23 Aralık
 15% 6 Ocak Lab final
 28101980

To minimize an expression one must cover all the 1-cells (= 1 points) of the expression with the smallest # of subcubes such that each subcube as large as possible

An SP expression from which no term or literal can be deleted without changing its logical value is called an IRREDUNDANT or IRREDUCIBLE form which is not unique in general.

Example :

 

Minimal PS expressions:

- form subcubes from the 0-points of the function
- Select largest and min. # of subcubes to cover the 0-points of f.
- Write corresponding min. SP expression which gives f'
- complement f' to find min. PS expr.

Example:

		1	
1		1	
1		1	
		1	

$F = CD + BC'D'$
minimal SP expression

0	0		0
	0		0
	0		0
0	0		0

$F'(A,B,C,D) = B'D' + C'D + CD'$
 $F(A,B,C,D) = (B+D)(C+D')(C'+D)$
minimal PS expression


Don't cares

- ORIGINS:
- Some input combinations may not appear at the input.
 - For some input combinations, related output may not be necessary.
- if there are k don't cares, 2^k different switching functions can be generated.
- "don't cares can be assumed" as 1 or 0

Example:

"BCD prime detector"

 0: not prime
1: not prime
then k is prime
if $k = k \cdot 1$



$f = 1$ if $b_0 b_1 b_2 b_3$ is prime

	b_3	b_2	b_1	b_0	f
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
	1	0	1	0	
	1	0	1	1	
	1	1	0	0	
	1	1	0	1	
	1	1	1	0	
	1	1	1	1	

	0	1	1	3	1	5
	5	1	1	3	1	7
b_3	d	d	d	d	d	d
	8	9	11	10		

$F(b_3, b_2, b_1, b_0) = b_2 b_0 + b_2' b_1$
min. SP expression

0	0		
0			0
d	d	d	d
0	0	d	d

$F' = b_2' b_1' + b_0' b_2$
 $F = (b_2 + b_1)(b_0 + b_2')$ → min PS exp.

Exercise: BCD → excess 3 translator EX-3

separately!

Definition: $f(x_1, x_2, \dots, x_n)$ is said to cover $g(x_1, x_2, \dots, x_n)$ $\{f \geq g\}$

if $g=1 \implies f=1$ or $g \implies f$
 g implies f
 g is an implicant of f

Example:

ABC	① $A'B'C$	③ $A'BC$	⑥ ABC'	⑦ ABC	$A'C$	AB	BC	f
000	0	0	0	0	0	0	0	0
001	1	0	0	0	0	0	0	1
010	0	1	0	0	0	0	0	1
011	0	1	0	0	0	0	0	1
100	0	0	0	0	0	1	0	1
101	0	0	0	0	0	1	0	1
110	0	0	0	0	1	0	1	1
111	0	0	0	1	1	1	1	1

①, ③, ⑥, ⑦, $A'C$, AB , BC are
 implicants of $f(A,B,C)$
 but BC is not an implicant
 of f .

Definition: Prime implicant

A prime implicant P of function f is a product term which is covered by f , such that the deletion of any literal from P results in a new product term which isn't covered by f (or is not an implicant of f)

Example: f : above.

Take ① $A'B'C \rightarrow BC$
 $A'B'C \rightarrow A'C$
 $A'B'C$ is not a prime implicant. (p.i.)

take ⑦ $ABC \rightarrow AB$ is implicant
 so ⑦ is not a prime implicant of f .

take $A'C \rightarrow A'$ since A' and C are not implicants of f , therefore $A'C$ is a p.i. of f .

Similarly AB and BC are p.i. of f .

\implies * Minimal SP expression is obtained by ^{properly} selecting p.i. of f .


Definition: Essential p.i.

A p.i. of f is essential p.i. if it covers at least one 1-point of f which is not covered by any other p.i.

 Example

03111980

$$f(x, y, z, w) = \sum (0, 4, 5, 7, 8, 9, 13, 15)$$



- a) ① \rightarrow ② are implicants of f .
- b) ⑦ \rightarrow ② are not prime implicants.
- c) ① \rightarrow ⑥ are prime implicants.
- d) ① is essential prime implicant.

$$f(x, y, z, w) = ① + ② + ③ = yw + x'w'z' + xy'z' \text{ unique min. SP expression.}$$

Procedure for minimal SP expression:

- ① Find all the prime implicants of the function determining the essential ones.
- ② Include all the essential prime implicants in the sum.
- ③ Remove the 1 points of f which are covered by essential prime implicants.
- ④ For the remaining 1 points select additional prime implicants so that the 1 points of f are covered completely.

Quine Mc Cluskey tabulation method

- ① Find the canonical SP expression of f.
- ② Arrange all minterms in groups such that all terms in the same group have the same # of 1's in their binary representation or the same # of prime variable.
- Start with the least # of 1's continue with groups of increasing # of 1's. (# of 1's in a minterm called index)
- ③ Compare another terms of the smallest index group with each term in the successive group whenever possible combine the two by means of the following equality in Boolean algebra:

$$\phi x + \phi' x = x$$

Repeat this by comparing each term in a group of index i with every term in the group of index i+1 until the table is finished. The combined term consists of original fixed representation with the different digit is replaced by a (-) 'dash'

- ④ The new terms generated will be again compared between them. A new term is generated by combining two terms which
 - a - Differ by only a single digit and
 - b - Whose (-)'s are in the same position

The process continues until no further combinations are possible, which gives the set of all prime implicants

Example:

$$f(a,b,c,d) = \sum (0,1,2,3,11,13,15)$$

- a'b'c'd - 0000
- a'b'c'd - 0001
- a'b'cd' - 0010
- a'b'cd - 0011
- a'b'c'd - 1011
- abc'd - 1101
- abcd - 1111

0	0000	✓	000- (0,1)	00-- (0,1,2,3) ← Same
1	0001	✓	00-0 (0,2)	
2	0010	✓		00-- (0,2,1,3) ← Same
3	0011	✓	00-0 (1,3)	
			001- (2,3)	
11	1011	✓	-011 (3,11)	
13	1101	✓		
			1-11 (11,15)	
15	1111	✓	11-1 (13,15)	

b'cd, acd, abd, a'b'

	0	1	2	3	11	13	15
(3,11) b'cd				X	X		
(11,15) acd					X		X
(13,15) abd						X	X
(0,1,2,3) a'b'	X	X	X	X			

Minimal expression:
 $f(a,b,c,d) = a'b' + abd + acd$

Example (Don't cares)

$$f(a,b,c,d) = \sum (1,5,10,13,14,15)$$

$$f(a,b,c,d) = \sum_d (0,2,7,9)$$

f	1	5	10	13	14	15
A	X					
B			X			
C			X		X	
D					X	X
E	X	X		X		
F		X		X		X

d(0)	0000	000-	(0,1)	-01 (1,5,9,13)
1	0001	00-0	(0,2)	--01 (1,9,5,13) (E)
d(2)	0010	0-01	(1,5)	-1-1 (5,7,13,15) (F)
5	0101	-001	(1,9)	=1-1 (5,13,7,15)
d(9)	1001	-010	(2,10)	
10	1010	01-1	(5,7)	
d(7)	0111	-101	(5,13)	
13	1101	1-10	(10,14)	
14	1110	1-01	(9,13)	
15	1111	-111	(7,15)	
		11-1	(13,15)	
		111-	(14,15)	(D)

no essential p.i
 E dominates A
 C dominates B
 ∴ A and B removed
 ∴ 5, 13, 14 deleted
 $f(a,b,c,d) = E \cdot C \cdot (D+F) = cd + acd'$
 and and or
 + abc
 + bd

Procedure of finding min. SP. expression:

- ① If in a column there is only a single X then the corresponding p.i. is essential include this in the min. SP expr. and remove all these columns and rows from the chart.
 - ② Def: Row K is said to dominate row M if K covers every column covered by M
 - ③ then if row K dominates row M, delete row M from the chart.
- Def: Column i is said to dominate column j if i has a (X) in every row in which j has a (X).
The dominating columns can be deleted from the chart.


1111980

Exercise $f(A,B,C,D) = \sum (0,1,5,7,8,10,14,15)$ Tabulation method minimization


Synthesis of single output combinational ckt.

$F = AB(C'+D) + AD'$

 i - If complemented input variables are available at the inputs:



 ii - if complemented (= primed) variables are not available.



① The functions of the following form
 $F_1 = AB$ $F_2 = A+B$
are called first-order expressions
Because they can be implemented by a single gate ckt. The obtained gating ckt. is called single level (= one level) ckt. (if complemented input variables are available)



② The functions: $F_3 = AB+C+D$ or $F_4 = (A+B)CD$
are called second order functions. The gating ckt. obtained from these functions are two-level ckt's. (if primed variables are available)

③ The functions $F_5 = (AB+C+D)E$, $F_6 = (A+B)CD+E$
are called third-order functions. Obtained ckt's are three level circuits.

➔ NAND/NOR
NOR/NAND realizations are not possible for any switching function.

NAND or NOR realisations of functions :

Ex 1

  

Rule for PS \rightarrow NOR realisation
 SP \rightarrow NAND

- ① Bracket each factor.
- ② Complement any literal which appears by itself in PS
- ③ If there is only one term such as

$(a+b+\dots+n)$ complement this term.
 $(a \cdot b \cdot \dots \cdot n)$

- ④ Replace (+) and (\cdot) operation by NOR operation (\downarrow)
 NAND (\uparrow) \uparrow means NOR

Ex: $F = (A+B)(C+D)$

- ① $(A+B)(C+D)$
- ② -
- ③ -
- ④ $(A \downarrow B) \downarrow (C \downarrow D)$

Ex: $F = A+B+C+D$

- ① $(A+B+C+D)$
- ② -
- ③ $(A+B+C+D)'$
- ④ $(A \downarrow B \downarrow C \downarrow D)'$


Rules for SP \rightarrow NOR

- ① Bracket each term.
- ② Complement each literals of each product unless the product consisted of only one literal.
- ③ Replace +, \cdot by \downarrow (NOR)
- ④ Complement entire function
- ⑤ If SP form has only one term don't complement it.

(NOTE: Does not give a two-level ckt in general)

$F = ab + cde$

 - ① $(ab) + (cde)$
- ② $(a'b) + (c'd'e')$
- ③ $(a' \downarrow b') \downarrow (c' \downarrow d' \downarrow e')$
- ④ $[\dots]'$



$F = ab + c$

- ① $(ab) + c$
- ② $(a'b) + c$ \leftarrow don't complement.
- ③ $(a' \downarrow b') \downarrow c$
- ④ $[(a' \downarrow b') \downarrow c]'$
- ⑤ -

Rules for PS \rightarrow NAND

- ① Bracket each term.
- ② Complement each literals of each factor unless the factor consisted of only one literal.
- ③ Replace +, \cdot by / (NAND)
- ④ Complement entire function
- ⑤ If PS form has only one factor don't complement it.


(NOTE: Does not give a two level ckt in general)

$F = (A+B)(C+D)$

- ① $(A+B)(C+D)$
- ② $(A'+B')(C'+D')$
- ③ $(A'/B')/(C'/D')$
- ④ $[(A'/B')/(C'/D')]'$
- ⑤ -


$F = A(B+C)$

 - ① $(A)(B+C)$
- ② $(A)(B'+C')$
- ③ $(A)/(B'/C')$
- ④ $[(A)/(B'/C')]'$
- ⑤ -



Multiple Output cct's and Minimization :


Example :

 


$$y_1(A, B, C, D) = \sum (4, 6, 13, 14, 15, 11, 9)$$

$$y_2(A, B, C, D) = \sum (1, 3, 5, 7, 9, 13, 11, 10, 15)$$

 
$$y_3(A, B, C, D) = \sum (1, 3, 4, 5, 6, 7, 10, 11, 14, 15)$$



$$y_1 = AD + A'BD' + ABC$$

 

$$y_2 = D + ABC$$

 

$$y_3 = A'D + AC + AB$$


Complemented variables are available, using AND/OR gating cct. :

$$y_1 = 4 \text{ gates} + 11 \text{ gate inputs}$$


$$y_2 = 2 \text{ gates} + 5 \text{ gate inputs}$$

$$y_3 = 4 \text{ gates} + 9 \text{ gate inputs}$$

 
$$\text{for } y_1, y_2, y_3 : 10 \text{ gates} + 25 \text{ gate inputs}$$




$$F_1 = AD + \bar{A}BD' + ABC$$

 

$$F_2 = AD + \bar{A}D + ABC$$

 
 
$$F_3 = \bar{A}D + \bar{A}BD' + ABC + ABC$$



8 GATES + 23 INPUTS

Tabulation Method for Multiple output ckt's

$$F_1(a,b,c) = \sum(0,4,7)$$

$$F_2(a,b,c) = \sum(0,3,4)$$

$$F_3(a,b,c) = \sum(3,4,5,6,7)$$

performing an AND operation bit by bit between the TAG's of 0,4

If TAG of new term is equal to previous ones put a '✓' near odd terms. (delete them)

	abc	f ₁	f ₂	f ₃	TAG
	0 000 ✓	1	1	0	(0,4) -00 110
(A) *	4 100	1	1	1	(4,5) 10- ✓ 001
(B) *	3 011	0	1	1	(4,6) 1-0 ✓ 001
	5 101 ✓	0	0	1	(3,7) -11 001
	6 110 ✓	0	0	1	(5,7) 1-1 ✓ 001
(C) *	7 111	1	1	1	(6,7) 11- ✓ 001

unchecked terms are multiple output prime implicants (mopis)

	f ₁	f ₂	f ₃
	0 4 7	0 3 4	3 4 5 6 7
A	X		X
B		X	X
C	X		X
(0,4) D	X	X	X
E			X
F			X

To cover f₁ you have to take D then A or D and C D(A+D)C

$$f_2: DB(A+D)$$

$$f_3: (B+E)(A+F)F(C+E+F)$$

to cover f₁, f₂, f₃: D(A+D)C · DB(A+D) · (B+E)(A+F)F(C+E+F)

DCBF ← RESULT

$$F_1: DC = b'c' + abc$$

$$F_2: DB = b'c' + a'bc$$

$$F_3: FB = a + a'bc$$

Example:

$$F_1: \sum(0,4,7)$$

$$F_2: \sum(0,3,4)$$

$$F_3: \sum(3,4,5,6,7)$$

$$F_4: \sum(1,2)$$

MT I

Map Method to minimize multiple output ct.


Procedure

- i - Find all pi's of functions.
- ii - Find all possible products of functions, find their pi's.
- iii - Label all pi which are distinct in the table. (Starting from bottom to top)
- iv - Form pi table.

$$f_1(a,b,c) = \sum (0,4,6,7)$$

$$f_2(a,b,c) = \sum (0,3,5,7)$$

$$f_3(a,b,c) = \sum (0,3,4,6)$$

 

Exercise: Don't cares → 1 points

$$F_1(A,B,C) = \sum (0,4,7)$$

$$F_2(A,B,C) = \sum (0,3,4)$$

$$F_3(A,B,C) = \sum (3,4,5,6,7)$$

$$d = \sum (1,2)$$

answer: 7 gates 19 gates.

$$f_1: \begin{array}{l} b\bar{c} \\ a\bar{c} \\ (6,7) ab \end{array} \text{ (H)}$$

$$f_2: \begin{array}{l} \bar{a}b\bar{c} \\ bc \\ ac \end{array} \text{ (F), (G)}$$

$$f_3: \begin{array}{l} \bar{a}bc \\ b\bar{c} \\ a\bar{c} \end{array}$$

$$f_1f_2: \begin{array}{l} \bar{a}b\bar{c} \\ abc \end{array} \text{ (E)}$$

$$f_1f_3: \begin{array}{l} b\bar{c} \\ a\bar{c} \end{array} \text{ (C), (D)}$$

$$f_2f_3: \begin{array}{l} \bar{a}b\bar{c} \\ \bar{a}bc \end{array} \text{ (B)}$$

$$f_1f_2f_3: \bar{a}b\bar{c} \text{ (A)}$$

	f ₁				f ₂				f ₃			
	0	4	6	7	0	3	5	7	0	3	4	6
f ₁ : H(6,7)		X	X									
f ₂ : F(3,7) G(5,7)						X	X					
f ₁ f ₂ E(7)			X				X					
f ₁ f ₃ C(0,4) D(4,6)	X	X							X		X	X
f ₂ f ₃ B(3)						X				X		
f ₁ f ₂ f ₃ (0) A	X				X				X			

$$f_1: (A+C)(E+D)(H+D)(H+E)$$

$$f_2: A(F+B)G(E+G+E)$$

$$f_3: (C+A)B(C+D)D$$


AGBD(H+E) preferring H

$$f_1: ADH$$






$$f_3: BDA$$

$$f_2: ABG$$

Combinational Hazards :

 


Example :

     

Static hazards (Due to single input changes only)

 Example: $f(A,B,C,D) = \sum (2,6,9,11,13,14,15)$

$f(A,B,C,D) = AD + ABC + \bar{A}C\bar{D}$



$y_1, y_2, y_3, y_4, y_5, y_6$ → State of the network

$\bar{y}_1, \bar{y}_2, \bar{y}_3, \bar{y}_4, \bar{y}_5, \bar{y}_6$ → Next state of network

next state equations:

$\bar{y}_1 = A'$
 $\bar{y}_2 = D'$
 $\bar{y}_3 = C y_1 y_2$
 $\bar{y}_4 = ABC$
 $\bar{y}_5 = AD$
 $\bar{y}_6 = y_3 + y_4 + y_5$

ABCD: 0110
 state of ckt:
 $y_1=1, y_2=1, y_3=1, y_4=0, y_5=0, y_6=1$ } Present state
 111001

ABCD → 1110

next states:

$\bar{y}_1=0, \bar{y}_2=1, \bar{y}_3=1$
 $\bar{y}_4=1, \bar{y}_5=0, \bar{y}_6=1$

present state: 111001

next state: $\overset{*}{0}\overset{*}{1}\overset{*}{1}\overset{*}{0}1$

this is also 0 → 1

this variable is trying to change from 1 to 0

⇒ if $\bar{y}_i \neq y_i$ then y_i is trying to change its state

if $\tau_1 < \tau_4 \rightarrow 011001$ PS
 $01\overset{*}{0}\overset{*}{1}01$ NS

if $\tau_1 = \tau_4 \rightarrow 011101$
 010101


if $\tau_2 < \tau_1 \rightarrow 111101$
 $01\overset{*}{0}\overset{*}{1}01$

ABCD = 0110 111001

ABCD = 1110 111001

↓
 $\overset{*}{0}\overset{*}{1}\overset{*}{1}\overset{*}{0}1$
 ↓

ABCD : 0110
 ABCD : 1110

 


Definition: If x^i and x^j are adjacent input symbols and a switching function has the same value for both input symbols;

$$f(x^i) = f(x^j) = 1 \text{ (or } 0)$$

then a network which realizes that function f contains a STATIC hazard if a "0" (or "1") can appear temporarily on its output line when the input symbol is changed from x^i to x^j , or vice versa.

To eliminate static hazards due to single input changes: every pair of adjacent minterms must be covered by at least one selected prime implicant.

example:

 


$$F_1 = \bar{A}\bar{D} + \bar{B}\bar{D} + BCD + \bar{A}BC$$

→ $m_6 : 0110$
 → $m_7 : 0111$ } these two adjacent terms are not included in a prime implicant. Because of this a change of $m_6 \leftrightarrow m_7$ may give a static hazard. We must include them with addition of a redundant p.i.

If multiple input changes are allowed:

- i. Generalisation of static hazard.
- ii. Function hazard.

Example:

 

$$F = AD + BC + \bar{A}B + \bar{C}D$$

No static hazard due to single input changes.

But if there will be a change between $m_{15} \leftrightarrow m_5$ (two inputs are changed) there may be hazard.

We must include another redundant gate to eliminate this hazard: BD


Definition

If x^1 and x^0 are different input symbols a static hazard exists if $f(x^1) = f(x^0) = 1$ (or 0) and $f = 0$ (or 1) can appear temporarily when input symbol is changed x^1 to x^0 . This hazard may be eliminated by including in the SP expression of function f a prime implicant that covers both x^1 and x^0 , if such p.i. exists.

SEQUENTIAL CIRCUITS

Flip-flops

 - RS flip flop. (RS-FF)
- Triggered flip-flop (T-FF)
- JK flip flop
- Delay flip flop (D-FF)
- Gated latch flip flop (GLFF)



$\bar{y}' = \Psi(x^0, y^k)$

$\Psi \Rightarrow \bar{y} = x \cdot y'$

$\Psi(x^0, y^0) = y^0$

$\Psi(x^0, y^1) = y^0$

$\Psi(x^1, y^0) = y^1$

$\Psi(x^1, y^1) = y^0$

$\xi \Rightarrow z = x \cdot y$

$\xi(x^0, y^0) = z^0$

$\xi(x^0, y^1) = z^0$

$\xi(x^1, y^0) = z^0$

$\xi(x^1, y^1) = z^1$

09121980

Ψ :

x	y	\bar{y}
0	0	0
0	1	0
1	0	1
1	1	0

State transition table

ξ :

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

output table

x	y	\bar{y}	z
0	0	0	0
0	1	0	0
1	0	1	0
1	1	1	1

State table




ξ :

y	x=0	x=1
0	0/0	1/0
1	0/0	0/1

ξ :

y	x^0	x^1
y^0	y^0/z^0	y^1/z^0
y^1	y^0/z^0	y^0/z^1

State diagram

   

Example: MOD 3 counter

given $X = \{x^0, x^1\}$ input alphabet

$Y = \{y^0, y^1, y^2, y^3\}$ state alphabet

$Z = \{z_0, z_1, z_2, z_3\}$

$$\psi: \begin{array}{l|l} J_1 = y_2 x & J_2 = y_1 x \\ K_1 = y_2' + x & K_2 = y_1 x \end{array}$$

General next state equation of JK FF $\bar{y} = Jy' + K'y$

$$\bar{y}_1 = J_1 y_1' + K_1' y_1 = (x y_2) y_1' + (x + y_2)' y_1 = x y_1' y_2 + x' y_1 y_2$$

$$\bar{y}_2 = (x y_1') y_2' + (x y_1)' y_2 = x y_1' y_2' + x' y_2 + y_1' y_2$$

next state equations

$Y = \{y^0, y^1, y^3\}$

ψ :

x	y_1	y_2	\bar{y}_1	\bar{y}_2
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0

$\Rightarrow \psi$

x	y	\bar{y}
x^0	y^0	y^0
x^0	y^1	y^1
x^0	y^2	y^0
x^0	y^3	y^3
x^1	y^0	y^1
x^1	y^1	y^3
x^1	y^2	y^0
x^1	y^3	y^0

\bar{z} :

$$z_1 = x y_1 y_2'$$


$$z_2 = x y_1' y_2$$

$Z = \{z_0, z_1\}$

x	y_1	y_2	z_1	z_2
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

PS	NS		Out	
	x^0	x^1	x^0	x^1
y^0	y^0	y^1	z^0	z^0
y^1	y^1	y^3	z^0	z^1
y^2	y^0	y^0	z^0	z^2
y^3	y^3	y^0	z^0	z^0

state table

 




Design of synchronous sequential circuits

Design Procedure:

- i. Form a model from the word description of the problem. (Find state diagrams)(stable)
- ii. Simplify the state table
- iii. Make a state assignment
- iv. Decide the type of FF's and find input equations.
- v. Design the remaining necessary combinational ckt's

   Example: Single input - single output (x/z)




The circuit determines whether the input bits at four successive times constitute a valid BCD digit representation, when $z=0$ at the fourth clock time indicates that previous three inputs and present bit constitute a valid BCD representation. when $z=1$ it indicates an invalid BCD representation. z is to be zero at all other times. Least significant bit of the code words appears first in time.



PS	NS/output	
	x=0	x=1
a	b,0	c,0
b	d,0	e,0
c	f,0	g,0
d	h,0	i,0
e	j,0	k,0
f	l,0	m,0
g	n,0	p,0
h	a,0	a,0
i	a,0	a,1
j	a,0	a,1
⋮	⋮	⋮
p	a,0	a,1

d000 → 0
d001 → 1


d111 → 7

   

PS	I/Out NS	
	x=0	x=1
0	0,0	4,0
1	0,0	4,0
2	1,0	5,1
3	1,0	5,1
4	2,0	6,1
5	2,0	6,1
6	3,0	7,1
7	3,0	7,1
X		
X		

X Example: A clocked sequential ct. will be designed which will have an output of 1^{only} at the clock time coinciding with the third of a sequence of three 1's. The ct. will be provided a separate reset mechanism to place it in a starting state say q_i.

 
Input: 001101011011101011...
Output: 0000000000000100...



for (A)

	NS		OUT	
	x=0	x=1	x=0	x=1
q ₀	q ₀	q ₁	0	0
q ₁	q ₀	q ₁	0	0
q ₂	q ₀	q ₃	0	1
q ₃	q ₃	q ₃	0	0
q ₄	q ₄	q ₁	0	0

Another representation:

 

STEP 2 State minimization

Definition: Equivalent states: Two states p and q of a machine are said to be equivalent if for every input signals applied to machine starting from p and from q generates the same output symbols and results in equivalent next states.

Example: Look at valid BCD checker.

PS	NS		x=0	x=1
	x=0	x=1		
0	0	4	0	0
1	0	4	0	0
2	1	5	0	1
3	1	5	0	1
4	2	6	0	1
5	2	6	0	1
6	3	7	0	1
7	3	7	0	1

- Ⓒ 4 and 5 equivalent
- Ⓐ 0 and 1 equivalent
- Ⓑ 2 and 3 equivalent
- Ⓓ 6 and 7 equivalent
- Ⓐ; (0,1)
- Ⓑ; (2,3)
- Ⓒ; (4,5)
- Ⓓ; (6,7)

PS	NS		OUT	
	x=0	x=1	x=0	x=1
A	A	C	0	0
B	A	C	0	1
C	B	D	0	1
D	B	D	0	1

} States C, D are equivalent too. (C,D): a

Partitioning algorithm: (only for completely specified m/c.)

i. Partition the set of all states into sets such that all members of a set have identical output rows in the state table.

$$S1 = \{a, b, c, d, e, f, g, h, l\}$$

$$S2 = \{i, j, k, m, n, p\}$$

ii. Under each state for each input symbol record the number of the set of which the next state is a member.

$$S1 = \{a, b, c, d, e, f, g, h, l\}$$

1, 1 1, 1 1, 1 1, 2 2, 2 1, 2 2, 2 1, 1 1, 1

$$S2 = \{i, j, k, m, n, p\}$$

1, 1 1, 1 1, 1 1, 1 1, 1

iii. Divide existing state sets so that all members of a new state set possess the same subscripts. When no new sets are formed the algorithm terminates, if new sets are formed repeat step ii.

$$S1 = \{a, b, c, h, l\}$$

1, 1 2, 3 2, 3 1, 1

$$S2 = \{d, f\}$$

1, 4 1, 4

$$S3 = \{e, g\}$$

4, 4 4, 4

$$S4 = \{i, j, k, m, n, p\}$$

1, 1 1, 1 1, 1 1, 1 1, 1 1, 1

Now repeat step ii; step iii:

$$S1 = \{a, h, l\}$$

2, 2 1, 1 1, 1

$$S2 = \{b, c\}$$

3, 4 3, 4

$$S3 = \{d, f\}$$

$$S4 = \{e, g\}$$

$$S5 = \{i, j, k, m, n, p\}$$

Again repeat:

$$A \rightarrow \{a\}$$

$$B \rightarrow \{h, l\}$$

$$C \rightarrow \{b, c\}$$

$$D \rightarrow \{d, f\}$$

$$E \rightarrow \{e, g\}$$

$$F \rightarrow \{i, j, k, m, n, p\}$$

we have started with a m/c which has 15 states and arrived a m/c which has 6 states. (Performing the same work)

To the top of the page.

	NS		OUT		
	x=0	x=1	x=0	x=1	
A	C	C	0	0	minimal state equivalent of valid BCD checker.
B	A	A	0	0	
C	D	E	0	0	
D	B	F	0	0	
E	F	F	0	0	
F	A	A	0	1	

*There is no minimal state for incompletely specified m/c.

STEP 3: STATE ASSIGNMENT

if $m = \# \text{ of states}$, to realize this m/c, let $p = \text{min} \# \text{ of required FF's}$.

$$P = \lceil \log_2 m \rceil \quad \lceil a \rceil = \text{smallest integer equal to or greater than } a.$$


If $2^{p-1} \leq m \leq 2^p$ satisfied then $\frac{2^p!}{(2^p - m)!}$ different assignments can be given to the states

State Assignment Rules

Rule I @ Check for rows of the state table which have identical next state entries in every column. Such rows should be given adjacent assignments. If possible next state entries in these rows should be given adjacent assignments according to rule II

@ Check for the rows of the ST which have the same next state entries but in different column order such that rows should be given adjacent assignments if the next state entries can be given adjacent assignments.

	x=0	x=1	x=0	x=1
A	B	C	0	0
B	D	E	0	0
C	E	D	0	0
D	F	G	0	0
E	G	F	0	0
F	A	A	1	0
G	A	A	0	1

 

- Rule Ia: assign adjacent codes for F and G.
- Rule Ib: DE must be adjacent if FG adjacent.
- Rule Ic: BC must be adjacent if DE adjacent.

Rule I: Rows with identical next state entries in some, but not at all, columns should be given adjacent assign. with rows having more identical columns having the higher priority.

	x	x	x	x
A	A	B	M	D
D	A	M	M	M

Rule II: Next state entries for a given row should be given adjacent assignments.

Rule III: Assignments should be done so as to simplify the output expressions.

STEP 4: FF INPUT EQUATIONS

Without considering the state assignment rules; let;


- A = 000
- B = 100
- C = 010
- D = 101
- E = 011
- F = 001

	NS		OUT	
	x=0	x=1	x=0	x=1
A	C	C	0	0
B	A	A	0	0
C	D	E	0	0
D	B	F	0	0
E	F	F	0	0
F	A	A	0	1


PS	NS		OUT		
	y ₃ y ₂ y ₁ x=0	y ₃ y ₂ y ₁ x=1	x=0	x=1	
000	010	010	0	0	unused state table
100	000	000	0	0	
010	101	011	0	0	
101	100	001	0	0	
011	001	001	0	0	
001	000	000	0	1	
110	Not used (d)				
111	Not used (d)				

$d = \sum(6, 7, 14, 15)$

$\bar{y}_1 = x'y_1y_3 + x'y_2y_3$

 



$z = \sum 9 = xy_1'y_2'y_3$

 

3 FF:

- y₁: JK FF
- y₂: SR FF
- y₃: T FF

y → ȳ	J	K	S	R	T	G	L
0 → 0	0	d	0	d	0	0	d
0 → 1	1	d	1	0	1	1	1
1 → 0	d	1	0	1	1	1	0
1 → 1	d	0	d	0	0	d	1

  

$J_1 = x'y_2y_3'$


$K_1 = x + y_3'$

$S_2 = y_1'y_2'y_3'$

$R_2 = y_3 + x'y_2$


$T_3 = y_2y_3' + xy_2'y_3 + y_1'y_2'y_3$

$z = xy_1'y_2'y_3$

 



Definition: A system where not all the output sequences and/or next states are specified for given input sequences.

	NS		OUT	
	x=0	x=1	x=0	x=1
I ₁	2	I ₂	1	0
I ₂	2	I ₁	1	1
2	I ₁	3	1	0
3	I ₁	2	1	1

 

Apply partitioning method (I₁, 2), (I₂, 3)
(A) (B)

PS	NS		OUT	
	x=0	x=1	x=0	x=1
A	A	B	1	0
B	A	A	1	1

  

(A): 01100
(B): 01010
↑ applicable
↑ not applicable

Starting state in m/c I say is 1
Starting state in m/c II is (either I₁ or I₂) say I₁
apply X: 00110 to both of m/c and check results.

X = 001100
I = z: 11dd11
II = z: 110011

Definition: Applicable input sequence I_s

i) An applicable input sequence to a system S with s as its starting state.

If and only if I_s leads to a specified next state after each input of the sequence except possibly the last.

Definition: State t of a system T is said to cover state s of a system S if and only if for all I_s applied to the system S starting in state s and to system T starting in state t, the outputs of T are the same as the outputs of S whenever the latter is specified.

I_s: 010110

Output T: 111110 - starting state t
" S: 11d1d0 - starting state s.
then t covers s "t>s"

Definition: System T is said to cover system S iff for every state s in S there exist a state t in T such that t>s

State reduction: given S find system T having smaller # of states than S and satisfy T>S

30/12/1980

S → T
T > S

1. Computation of maximal compatible sets.
2. Finding the reduced state m/c using the compatible sets.

Definition: Compatible output sequences: Two output sequences are said to be compatible if the corresponding outputs of two sequences are equal whenever they are both specified.

Let Z_s: output sequence of length r, obtained by an applicable input sequence I_s of length r, starting state s.


Definition: Compatible states (i, j) two states i and j of system S are said to be compatible iff the output sequences Z_i^r and Z_j^r are compatible for all input sequences I_i^r and I_j^r.

Definition: n mutually compatible states: A set of n states of system S is said to be mutually compatible iff every pair of the states of the set is compatible.

{i, j, k}

Definition: Maximal compatible states: a set of n mutually compatible states is said to be a set of maximal compatible states iff it does not form a proper subset of another set of states that is mutually compatible.

Example:

 

PS	NS		OUT	
	x=0	x=1	x=0	x=1
1	2	1	0	1
2	3	d	0	d
3	d	4	d	0
4	5	d	0	d
5	d	1	0	1

Find compatible state pairs;

- (1, 5) are compatible
- (1, 3) not compatible
- (1, 2) are compatible if 2 and 3 are compatible
- (1, 2) → (2, 3)
↑ implied state pair.

Paul Ungler Tabulation method to find maximal compatible states sets:

- i. implication table
- ii. mutually compatibilities table \rightarrow MC's

implication table

2	(2,3)			
3	X	✓		
4	(2,5)	(3,5)	✓	
5	✓	✓	X	✓
	1	2	3	4

mutually compatibilities table

4	(4,5)								
3	(4,5) (3,4)								
2	(4,5) (3,4) (2,5) (2,3)								
1	(4,5) (3,4) (2,5) (2,3) (1,5) (1,4) (1,2) (1,2,5) (1,4,5)								

MC's: (3,4) (2,3) (1,2,5) (1,4,5)
maximal compatible state sets.

S : original m/c $S_1, S_2 \dots S_j$
 Δ : m/c obtained by taking all maximal compatibilities as its states.
 states are: $d_1, d_2 \dots d_n$

T : reduced m/c of states $P_1, P_2 \dots P_k \quad k \leq n$

$T > S$ obtained by taking some MC's sets of S

H = upper bound of $k \quad \min\{j, n\}$

ex: upper bound of $\min\{6, 5\} = 5$

$k \leq H$

The selected set of MC's to form the m/c T of states $P_1, P_2 \dots P_k$ must satisfy the followings:

I: Completeness: The union of states in all P sets must contain all the states of the original system.

II: Consistency: (Closure) Any set of next states P produced by an input symbol applied to the system S with any of the states of a P set as a starting state must be either a P set or a subset of a P set of T .

Example:

	00	01	10	11	00	01	10	11
0	0	1	3	2	d	d	d	d
1	1	2	4	3	d	d	d	d
2	2	3	5	4	0	0	0	0
3	3	4	0	5	1	1	1	1
4	4	5	1	0	0	0	0	0
5	5	0	2	1	d	d	d	d

1	(1,2) (3,4)				
2	(1,3) (3,5)	(2,3) (4,5)			
3	(1,4) (2,5)	(2,4) (4,0)			
4	(1,5) (3,1)	(2,5)	(3,5)		
5	(1,0)	(2,0)	(3,0)	(4,0)	(5,0)
	0	1	2	3	4

4	X
3	(3,5)
2	(3,5) (2,5) (2,4)
1	(3,5) (2,5) (2,4) (1,5) (1,4) (1,3) (1,3,5)
0	(3,5) (2,5) (2,4) (1,5) (1,4) (1,3) (1,3,5) (0,4) (0,3) (0,2) (0,2,4)

MC's: (2,5) (1,4) (1,3,5) (0,2,4) (0,3)

	P_1	P_2	P_3
	(2,5)	(1,4)	(0,3)
00	(2,5)		
01	(3,1) X		
10	(5,2)		
11	(4,1)		

III: Minimality: The number of states of $T (=k)$
 $k \leq H$

Lower bound $U = \max\{l_1, l_2, \dots, l_m\}$ where l_j is a set of maximally incompatible set.

4	(4,5) ^{not compatible}
3	(4,5) (3,4)
2	(4,5) (3,4) (2,3)
1	(4,5) (3,4) (2,3) (1,2)
0	(4,5) (3,4) (2,3) (1,2)

maximal incompatible sets of m/c S

$$U = \max\{2, 2, 3, 3\}$$

$$2 \leq k \leq 5$$

Example :

PS	NS		OUT	
	x=0	x=1	x=0	x=1
1	2	6	0	0
2	3	1	1	1
3	d	4	d	0
4	d	5	d	0
5	3	d	1	d
6	7	d	1	d
7	d	8	d	0
8	d	d	d	1

Answer:
3 state m/c

Example :

	NS, OUT			
	x ¹	x ²	x ³	x ⁴
1	2,d	3,0	d,d	4,d
2	3,0	5,0	d,d	d,d
3	4,d	6,d	3,d	d,d
4	5,d	3,0	d,d	1,d
5	d,d	6,0	d,d	d,d
6	d,d	d,1	4,d	2,d

Answer:
4 state m/c

- MC's (0,2,4)(1,3,5)(2,5)(1,4)(0,3)
- MC's (4,5)(3,4)(2,3)(1,2)(0,5)(0,1)

H=5

L = max(2,2,2,2,2,2) = 2

5 ≤ k ≤ 2

- Completeness
- Consistency
- Minimality

(0,2,4)(1,3,5)(1,4)(2,5)(0,3)
more stable (0,2,4)(1,3,5)(2,5)

Take:

- (0,2,4)(1,3,5)

(0,2,4)(1,3,5) = {0,1,2,3,4,5}

Table of the next states :

		PS		NS (obtained from original table)
		(0,2,4)	(1,3,5)	
INPUTS	0,0	(0,2,4)	(1,3,5)	
	0,1	(1,3,5)	(2,4,0)	
	1,0	(3,5,1)	(4,0,2)	
	1,1	(2,4,0)	(3,5,1)	

(0,2,4) = A
(1,3,5) = B
Consistency requirement is obtained (since # of NS are equal to # of PS in the table)

PS	NS				OUT			
	00	01	10	11	00	01	10	11
A	A	B	B	A	0	0	0	0
B	B	A	A	B	1	1	1	1

Example :

PS	NS				OUT			
	00	01	10	11	00	01	10	11
1	3	4	2	5	d	d	d	d
2	4	d	d	d	d	d	d	d
3	6	7	6	8	d	d	d	d
4	7	d	d	8	d	d	d	d
5	8	7	d	d	d	d	d	d
6	1	1	1	1	00	01	00	10
7	1	1	1	1	01	01	01	10
8	1	1	1	1	10	01	10	10

Find Maximal Compatible's (MC's) :

- (1,2,3,6)(1,2,3,7)
 C₃(1,2,3,8)(1,4,6) C₄
 C₅(1,4,7)(1,4,8) C₆ ← No of Comp. state.
 C₇(1,5,6)(1,5,7) C₈
 C₉(1,5,8)

Maximal Incompatible's (MIC's) :

- (6,7,8)(3,4,5)(2,4,5)

H = min(8,9) = 8

L = max(3,3) = 3

8 ≥ k ≥ 3

interesting thing is that the # of MC's are greater than the # of states of m/c

- C₁C₅C₉ = C₁UC₅C₉ = {1,2,...,8}
 C₁UC₆UC₈ = {1,2,...,8}
 C₂UC₄UC₉ = {1,2,...,8}
 C₂UC₆UC₇ = {---}
 C₃UC₇UC₅ = {---}
 C₅C₄C₈ = {---}

	(1,2,3,6)	(1,4,7)	(1,5,8)	(3,7,1)	(1,3,8)
00	(3,6,1)	(3,7,1)*	(1,3,8)*	(3,6,1)	(3,6,1)
01	(1,4,7)	(1,4)	(1,4,7)	(4,7,1)	(4,7,1)
10	(1,2,6)	(1,2)	(1,2)	(2,6,1)	(2,6,1)
11	(1,5,8)	(1,5,8)	(1,5)	(5,8,1)	(5,8,1)

Since (3,7,1) is neither equal nor a subset of PS, consistency requirement is not obtained [(1,3,8) is also]

For all other combinations satisfying completeness, not possible to satisfy consistency!

If we take C₁C₅C₉ we must take

C₁C₅C₉ + (3,7,1) + (1,3,8) So we have to add

to present states C₂ and C₃ and also find the NS's of C₂, C₃. Thus our m/c becomes a 5 state m/c and satisfies